One pad; equivalent feedback circuit

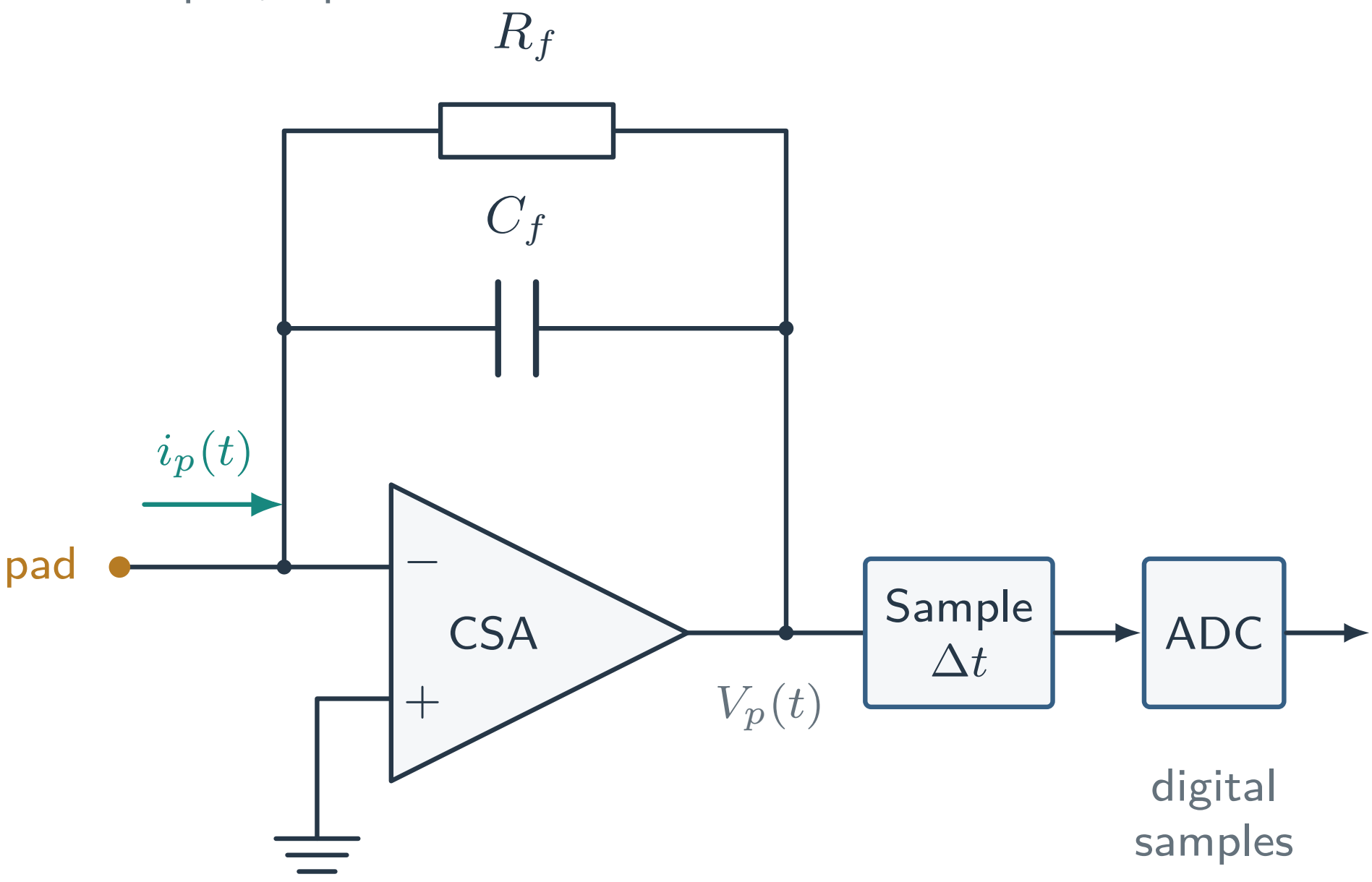

C_f: charge integration

R_f: effective MOS feedback resistance

Feedback discharge time: $\tau_f = R_f C_f$